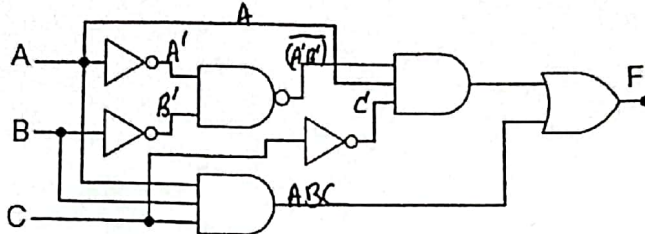


Digital Logic Design
Quiz# 3

Solution

1. For the circuit shown below, write down the output F as a function of the inputs A, B, C. [4]



2. Reduce the function obtained in Q. 1 to minimized SOP form. [3]
3. Draw the minimized function (Q. 2) using AND, OR and NOT gates. [3]

(i). $F = (\overline{A} \overline{B}) A' C' + ABC$

(iii)

(ii). $F = (A' B')' AC' + ABC$

Apply De Morgan's Theorem.

$$= ((A')' + (B')') AC' + ABC$$

$$= (A + B) AC' + ABC$$

$$= A \cdot AC' + ABC' + ABC$$

$$= AC' + ABC' + ABC$$

$$= AC' + AB(C + C')$$

$$\boxed{= AC' + AB}$$

$$\therefore (A')' = A$$

$$\therefore A \cdot A = A$$

$$\therefore C + C' = 1$$

