

**FoE Practice Test (Fall 2024)**  
**SE201T – Digital Logic Design**

Name: Solution  
Time allowed: 1 hour

Roll No.: \_\_\_\_\_  
Maximum Marks: 20

**Instructions**

- This test exam will assess your CLOs as per OBE.
- It is a **CLOSED BOOK/NOTES** exam.
- Part I has **TWO (2) questions/problems with a,b part** for which you are required to provide the solution in the given space.
- If you are found cheating or helping others cheat, your test will be cancelled and disciplinary action will be taken.

**CLOs**

- Apply the concept of different number systems and representations, to perform number system conversions and arithmetic operations.
- Apply the concepts of Boolean algebra and logic simplification to realize simplified designs of combinational and sequential circuits.
- Demonstrate the design of sequential circuits from their respective finite state machine representations.


Part I				Total (20)
Q1a – CLO1 (5)	Q1b – CLO2 (5)	Q2a – CLO2 (5)	Q2 – CLO2 (5)	

Instructor: Ms. Aqsa Khalid  
Teaching Assistant: Ms. Areesha Sami

Signature: \_\_\_\_\_

**PART I**

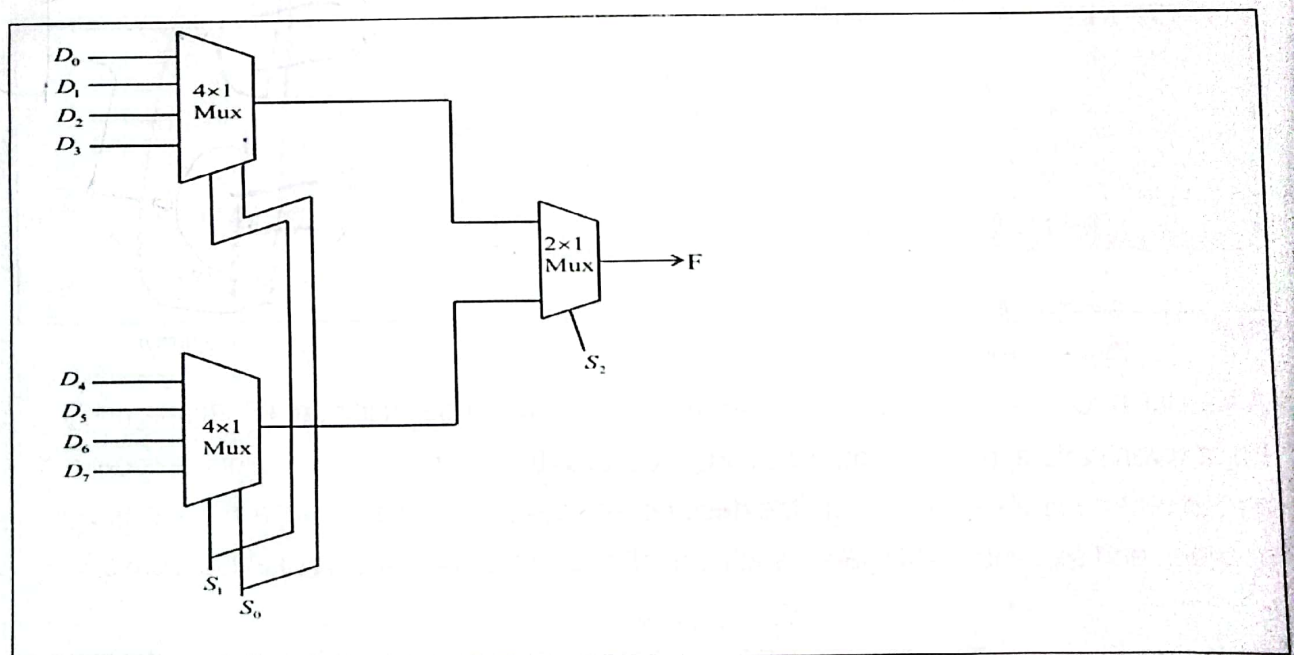**Q1) a-** (5 marks)  
Design an optimized solution for 8-to-1 line multiplexer using 4-to-1 and 2-to-1 line multiplexer.






Q1) b-

(5 marks)


A majority circuit is a combinational circuit whose output is equal to 1 if the input variables have more 1's than 0's. The output is 0 otherwise.

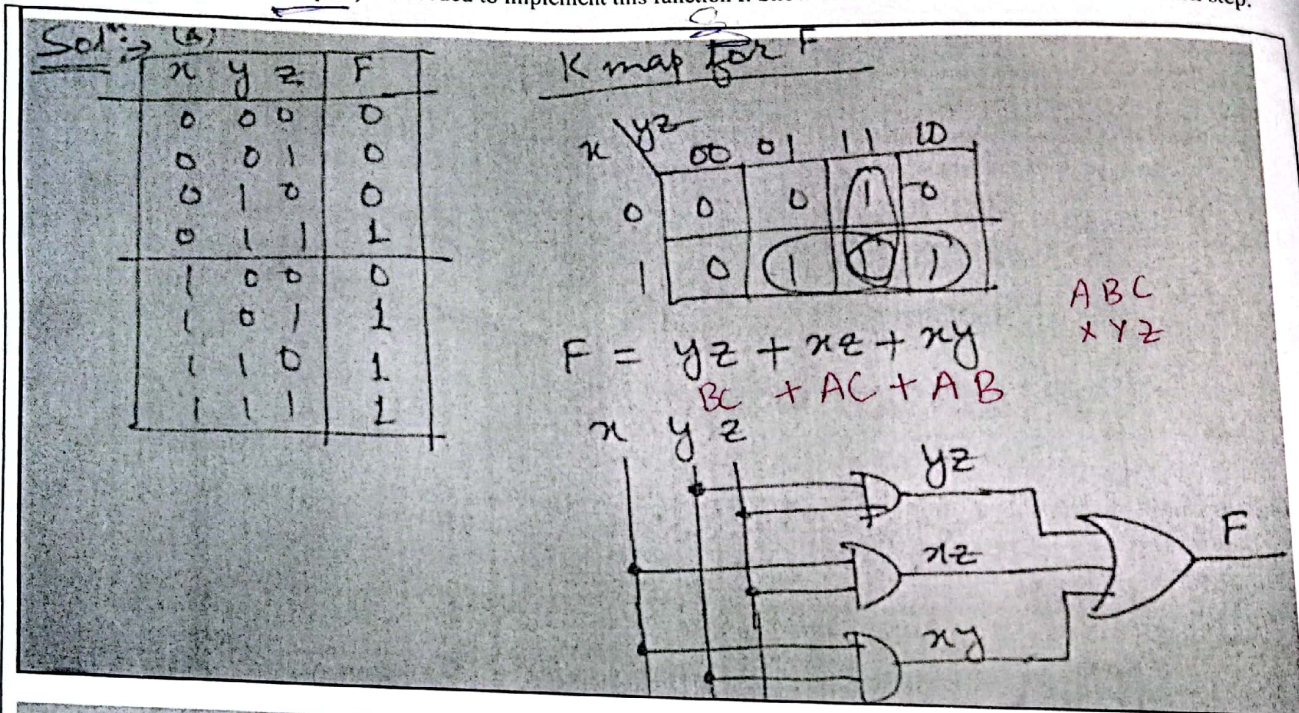- (a) Design a 3 input majority circuit by finding the circuit's truth table, Boolean equation, and a logic diagram.  
 (b) How many nand gates (2 inputs) are needed to implement this function f. Show derivation with law names also at each step.



(b)  $F = \{yz + zx + xy\}'$   
 $= \{(yz)' \cdot (zx)' \cdot (xy)'\}$

we have 3 no. of 2 input NAND gate.

 

Q2) a-

2-4-6-8  
 3-10-6-11

(5 marks)

A special 4-to-6-line decoder is to be designed. The input codes used are 000 through 101. For a given code applied, the output  $D_i$ , with  $i$  equal to the decimal equivalent of the code, is 1 and all other outputs are 0. Design the decoder with a 2-to-4-line decoder, a 1-to-2-line decoder, and six 2-input AND gates, such that all decoder outputs are used at least once.

4-10-6



$2^4 = 16$   
 $4 - 16$


4 to 6

2-to-4 line decoder and 2

tion of 2-to-4 line

$A_3$	$A_2$	$A_1$	$A_0$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	0	0	1	0
0	0	1	0	0	0	0	1	0	0	0
0	0	1	1	0	0	1	0	0	0	0
0	1	0	0	0	0	1	0	0	0	0
0	1	0	1	0	1	0	0	0	0	0
0	1	1	0	1	0	0	0	0	0	0
0	1	1	1	1	0	0	0	0	0	0

decoder,

 

Q2) b-

A combinational circuit is defined by the following three Boolean functions:

$$F_1 = \overline{X + Z} + XYZ$$

$$F_2 = \overline{X + Z} + \bar{X}YZ$$

$$F_3 = X\bar{Y}Z + \overline{X + Z}$$

Design the circuit with a decoder and external OR gates.

$$F1 = \overline{X} + \overline{Z} + XYZ$$

$$F2 = \overline{X} + \overline{Z} + \overline{X}YZ$$

$$F3 = X\overline{Y}Z + \overline{X} + \overline{Z}$$

First we express the functions in minterm canonical form by expanding the second term with the missing literal.

$$\text{i.e. } F1 = \overline{X} + \overline{Z} + XYZ$$

$$= (\overline{X} \cdot \overline{Z}) + (XYZ)$$

$$= (\overline{X} \cdot \overline{Z})(Y + \overline{Y}) + (XYZ) \quad (\because Y + \overline{Y} = 1)$$

$$= \overline{X}Y\overline{Z} + \overline{X}\overline{Y}\overline{Z} + XYZ$$

$$\therefore F1 = \sum m(0, 2, 7)$$

Step 2 of 4

$$F2 = \overline{X} + \overline{Z} + \overline{X}YZ$$

$$= (\overline{X} \cdot \overline{Z}) + \overline{X}YZ$$

$$= (\overline{X} \cdot \overline{Z})(Y + \overline{Y}) + (\overline{X}YZ) \quad (\because Y + \overline{Y} = 1)$$

$$= \overline{X}Y\overline{Z} + \overline{X}\overline{Y}\overline{Z} + \overline{X}YZ$$

$$F2 = \sum m(0, 2, 3)$$

Step 3 of 4

$$F3 = X\overline{Y}Z + \overline{X} + \overline{Z}$$

$$= (X\overline{Y}Z) + (\overline{X} \cdot \overline{Z})$$

$$= (X\overline{Y}Z) + (\overline{X} \cdot \overline{Z})(Y + \overline{Y}) \quad (\because Y + \overline{Y} = 1)$$

$$= X\overline{Y}Z + \overline{X}Y\overline{Z} + \overline{X}\overline{Y}\overline{Z}$$

$$F3 = \sum m(0, 2, 5)$$

Step 4 of 4

The circuit is designed by using one 3-to-8 decoder.

