


1. A sequential circuit with two D flip-flops A and B, one input X, and one output Z is specified by the following input equations:

(b)

A	B	X	A ⁺	B ⁺	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

(c) Draw the state diagram.

[3]

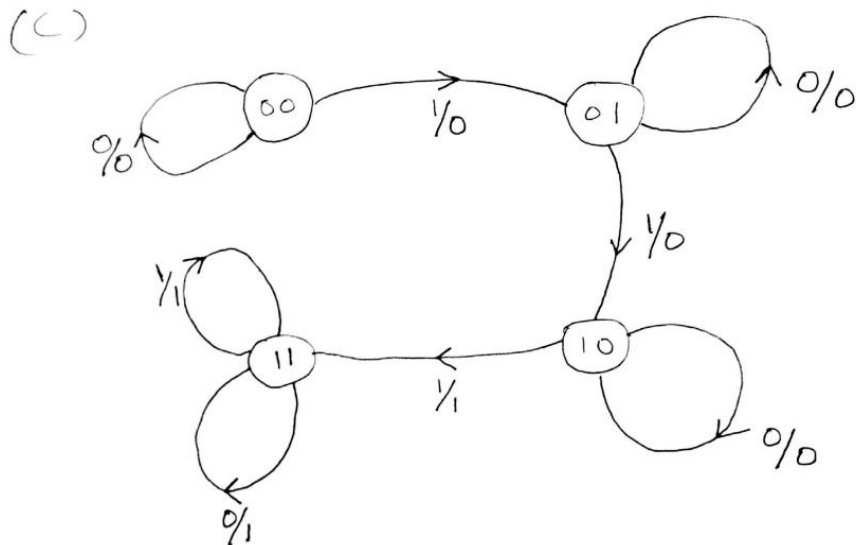

(d) Briefly describe the functionality of the circuit in your own words.

[1]

(d) This is a saturating 2-bit counter. It counts up when the input is high. The output is high when it reaches the saturation.