 



Q:

Determine the final output states over time for the following circuit, built from D-type gated latches:



At what specific times in the pulse diagram does the final output assume the input's state? How does this behavior differ from the normal response of a D-type latch?


Sol:

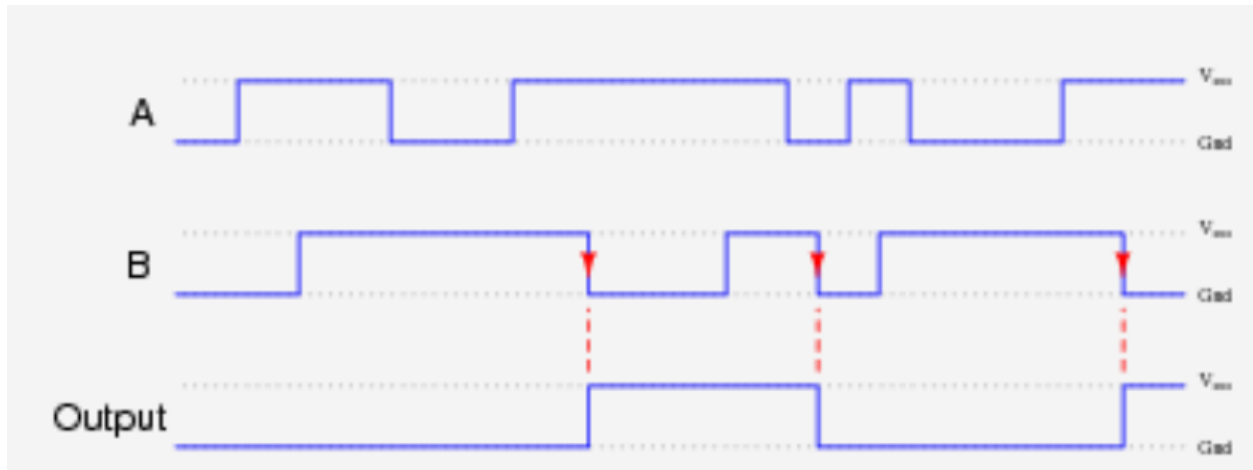


The final output assumes the same logic state as the input only when the enable input signal (B) *transitions* from “high” to “low”.

Q:

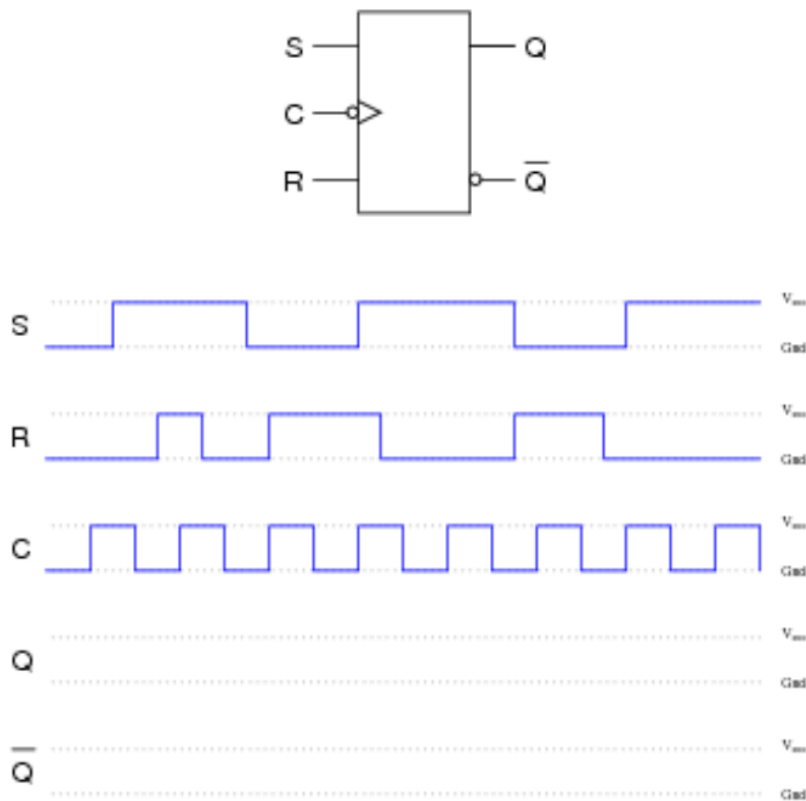Determine the output states for this S-R flip-flop, given the pulse inputs shown:



Ans:


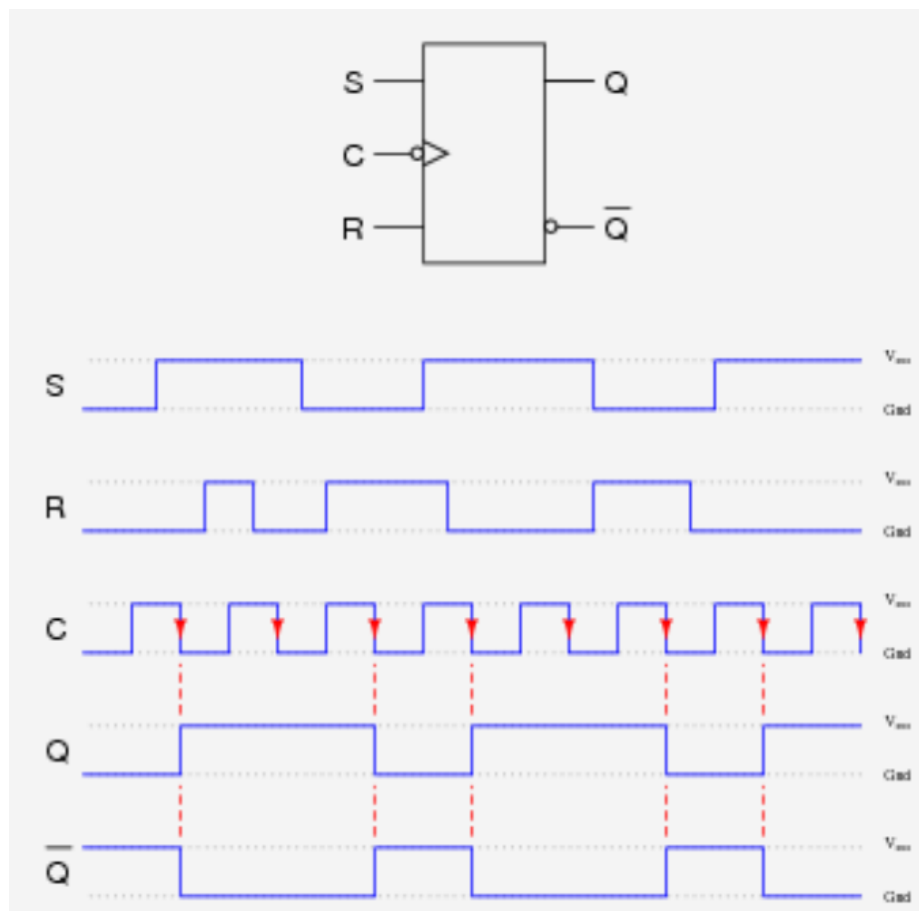


negative-edge-triggered SR flip-flop shows the output of the flip-flop when the clock pulse transitions from 1 to 0:

- **S = 1, R = 0:** Set
- **S = 0, R = 0:** Hold
- **S = 0, R = 1:** Reset
- **S = 1, R = 1:** Not allowed


Q:

  Determine the output states for this J-K flip-flop, given the pulse inputs shown:





Inputs			Outputs		Comments
J	K	CLK	Q	\bar{Q}	
0	0	\uparrow	Q_0	\bar{Q}_0	No change
0	1	\uparrow	0	1	RESET
1	0	\uparrow	1	0	SET
1	1	\uparrow	\bar{Q}_0	Q_0	Toggle

Ans:

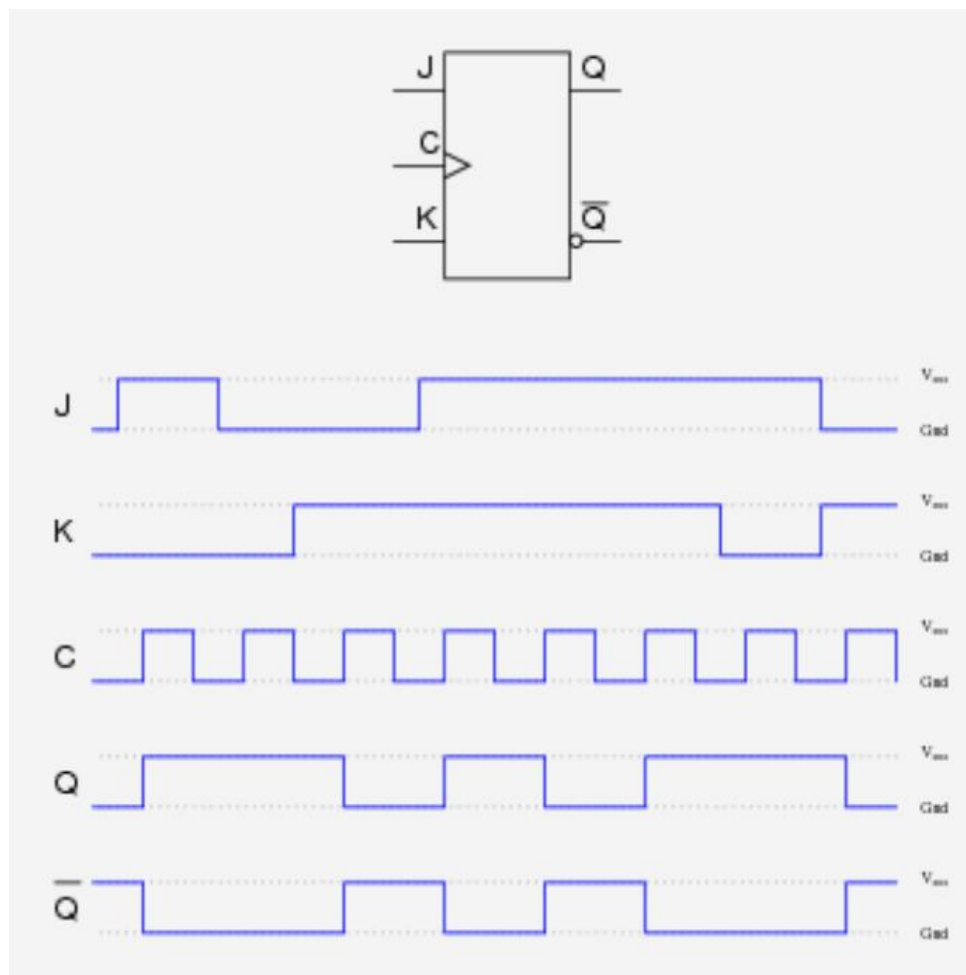


Q:

  Determine the output states for this D flip-flop, given the pulse inputs shown:





Sol:

C	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1


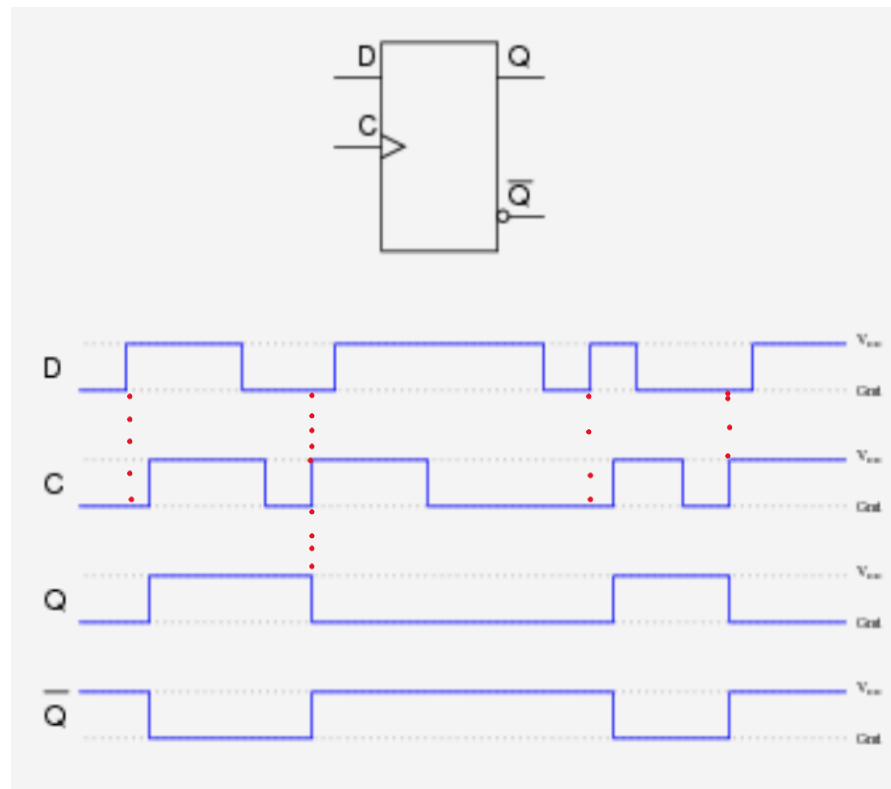


Q:

  Determine the output states for this J-K flip-flop, given the pulse inputs shown:



Sol:

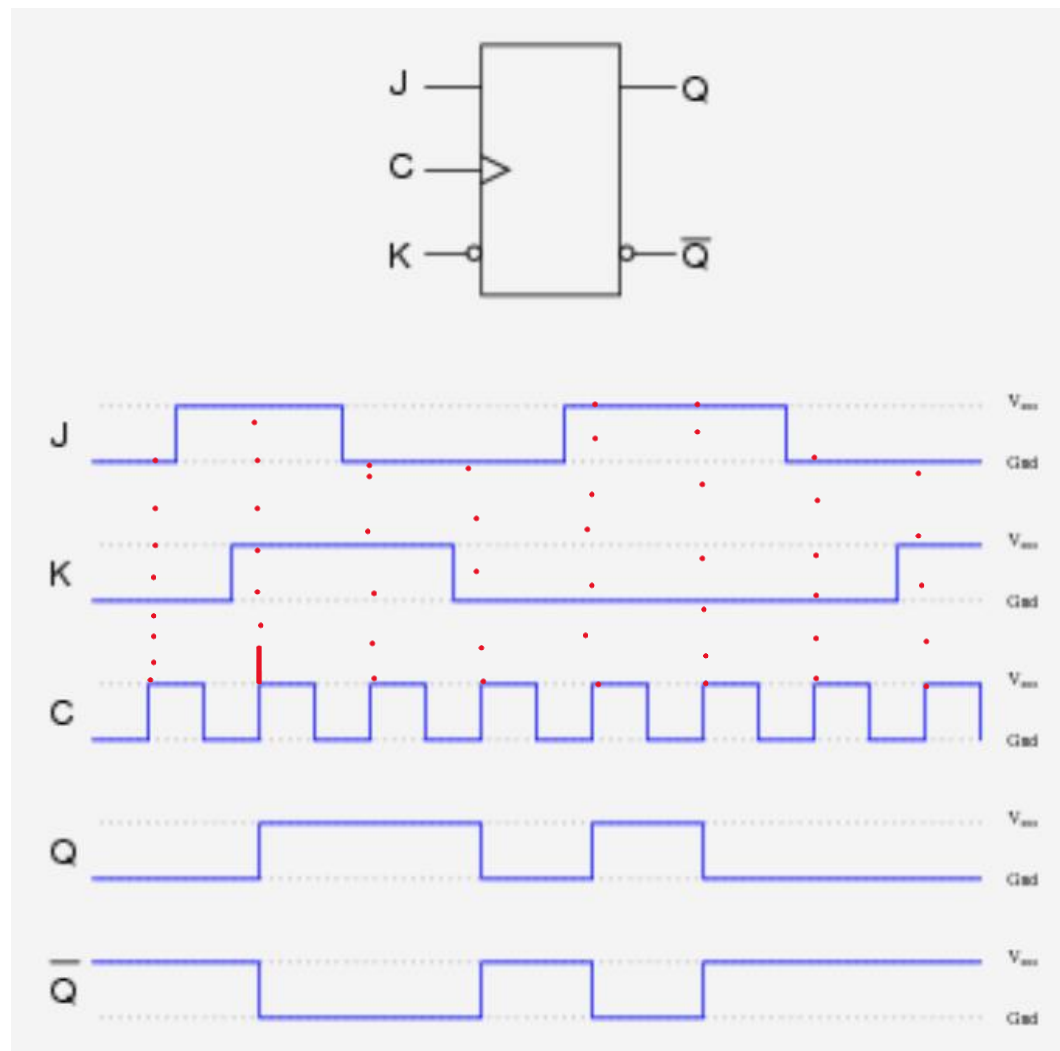 

Reference:

<https://www.allaboutcircuits.com/worksheets/flip-flop-circuits/#>